

## **Practical Manual for Basic Hardware Maintenance (COM223)**

**Level:** 200

**Course Code:** COM223

**Engr. Olasina, J. R.**  
**Department of Computer Engineering,**  
**School of engineering, Federal Polytechnic Ilaro,**  
**Ogun State, Nigeria**

**July, 2024**

## Workshop 1: Basic Electrical Theories and Ohm's Law

**Date:**

**Workshop Number:** 1

**Title:** Basic Electrical Theories and Ohm's Law

**Aim:** To understand and apply Ohm's Law in simple electrical circuits.

**Objectives:**

1. Verify Ohm's Law using different resistor values.
2. Calculate current, voltage, and resistance in a circuit.
3. Compare experimental results with theoretical predictions.

**Significance:** Understanding Ohm's Law is fundamental to all electrical and electronic circuit analysis.

**Theoretical Background:** Ohm's Law states that the current through a conductor between two points is directly proportional to the voltage across the two points.  $V=IR$   $V = IR$   $V=IR$ .

**Equipment:**

- Resistors
- Multimeter
- Breadboard
- Power supply
- Connecting wires

**Observation:** Record the voltage, current, and resistance for each circuit configuration.

**Diagram:** Draw the circuit diagram used in the experiment.

**Conclusion:** Discuss how the experimental results align with Ohm's Law.

**Precautions:** Ensure correct polarity of the power supply to prevent damage to the circuit components.

**Exercises:** Calculate the resistance needed to achieve a specific current in a circuit.

## Workshop 2: Thevenin's Theorem

**Date:**

**Workshop Number:** 2

**Title:** Thevenin's Theorem

**Aim:** To apply Thevenin's Theorem to simplify complex circuits.

**Objectives:**

1. Determine the Thevenin equivalent of a given circuit.
2. Analyze a complex circuit using its Thevenin equivalent.
3. Validate the theoretical results with experimental data.

**Significance:** Thevenin's Theorem simplifies the analysis of complex circuits by reducing them to a single voltage source and series resistance.

**Theoretical Background:** Thevenin's Theorem states that any linear electrical network can be replaced by an equivalent circuit consisting of a single voltage source and a series resistance.

**Equipment:**

- Resistors
- Multimeter
- Breadboard
- Power supply
- Connecting wires

**Observation:** Record the Thevenin equivalent voltage and resistance, and compare with the original circuit's behavior.

**Diagram:** Provide the circuit diagram before and after applying Thevenin's Theorem.

**Conclusion:** Explain how Thevenin's Theorem simplifies circuit analysis.

**Precautions:** Ensure all connections are secure to avoid measurement errors.

**Exercises:** Convert a given circuit into its Thevenin equivalent and predict the current for a given load.

## Workshop 3: Norton's Theorem

**Date:**

**Workshop Number:** 3

**Title:** Norton's Theorem

**Aim:** To verify Norton's Theorem in the analysis of electrical circuits.

**Objectives:**

1. Calculate the Norton equivalent of a circuit.
2. Analyze circuit behavior using its Norton equivalent.
3. Compare experimental data with theoretical expectations.

**Significance:** Norton's Theorem provides an alternative method to Thevenin's for simplifying circuits, using a current source and parallel resistance.

**Theoretical Background:** Norton's Theorem states that any linear electrical network can be reduced to an equivalent circuit with a single current source in parallel with a resistance.

**Equipment:**

- Resistors
- Multimeter
- Breadboard
- Power supply
- Connecting wires

**Observation:** Measure and record the Norton current and parallel resistance, and compare with the original circuit's behavior.

**Diagram:** Include the circuit diagrams before and after applying Norton's Theorem.

**Conclusion:** Discuss the practical applications of Norton's Theorem in circuit design.

**Precautions:** Double-check resistor values to ensure accuracy in calculations.

**Exercises:** Derive the Norton equivalent for a given circuit and calculate the load current.

## Workshop 4: Resistors in Series and Parallel

**Date:**

**Workshop Number:** 4

**Title:** Resistors in Series and Parallel

**Aim:** To study the behavior of resistors when connected in series and parallel configurations.

**Objectives:**

1. Measure the total resistance in series and parallel resistor networks.
2. Verify the relationship between individual and total resistances.
3. Compare experimental results with theoretical predictions.

**Significance:** Understanding resistor networks is essential for designing circuits with precise resistance values.

**Theoretical Background:** The total resistance in a series circuit is the sum of all resistances. In a parallel circuit, the reciprocal of the total resistance is the sum of the reciprocals of individual resistances.

**Equipment:**

- Resistors
- Multimeter
- Breadboard
- Connecting wires

**Observation:** Record the measured total resistance for both series and parallel configurations.

**Diagram:** Draw the series and parallel resistor network diagrams.

**Conclusion:** Explain how series and parallel resistor networks are used in practical circuit design.

**Precautions:** Ensure that all connections are tight to avoid errors in resistance measurement.

**Exercises:** Design a circuit that achieves a specific resistance using a combination of series and parallel resistors.

## Workshop 5: Logic Gates

**Date:**

**Workshop Number:** 5

**Title:** Logic Gates

**Aim:** To understand the operation of basic logic gates and their applications in digital circuits.

**Objectives:**

1. Construct and test basic logic gates (AND, OR, NOT) using ICs.
2. Verify the truth table for each logic gate.
3. Combine logic gates to create simple digital circuits.

**Significance:** Logic gates are the fundamental building blocks of digital electronics, used in everything from simple circuits to complex processors.

**Theoretical Background:** Logic gates perform basic logical functions that are fundamental to digital circuits. Each gate has a specific truth table that describes its operation.

**Equipment:**

- Logic gate ICs (e.g., 7400 series)
- Breadboard
- Connecting wires
- Power supply

**Observation:** Test and record the output of each gate for different input combinations.

**Diagram:** Include the circuit diagrams for each logic gate configuration.

**Conclusion:** Discuss how logic gates can be combined to create complex digital systems.

**Precautions:** Ensure correct pin connections to avoid damaging the ICs.

**Exercises:** Design a digital circuit using a combination of AND, OR, and NOT gates to solve a specific problem.



## Workshop 6: Active and Passive Components

**Date:**

**Workshop Number:** 6

**Title:** Active and Passive Components

**Aim:** To differentiate between active and passive components and understand their roles in electronic circuits.

**Objectives:**

1. Identify and categorize electronic components as active or passive.
2. Understand the function of each component in a circuit.
3. Analyze a circuit that includes both active and passive components.

**Significance:** Knowing the difference between active and passive components is essential for understanding how circuits work and how to troubleshoot them.

**Theoretical Background:** Active components (e.g., transistors, diodes) can amplify signals, while passive components (e.g., resistors, capacitors) cannot.

**Equipment:**

- Assorted resistors, capacitors, and inductors
- Transistors and diodes
- Multimeter
- Breadboard

**Observation:** Record the behavior of the circuit when active and passive components are included.

**Diagram:** Provide a diagram showing the placement of active and passive components in the circuit.

**Conclusion:** Explain the roles of active and passive components in circuit design.

**Precautions:** Handle transistors and diodes carefully to avoid damaging them with static electricity.

**Exercises:** Design a simple amplifier circuit using a transistor and analyze its performance.

## Workshop 7: Introduction to Computer Systems

**Date:**

**Workshop Number:** 7

**Title:** Introduction to Computer Systems

**Aim:** To explore the basic components and architecture of a computer system.

**Objectives:**

1. Disassemble and reassemble a computer system.
2. Identify key components (CPU, RAM, storage devices, etc.).
3. Understand the function of each component within the system.

**Significance:** A deep understanding of computer system components is crucial for hardware maintenance and troubleshooting.

**Theoretical Background:** A computer system consists of several key components, each playing a specific role in processing and storing data.

**Equipment:**

- Computer system
- Screwdriver set
- Antistatic wrist strap

**Observation:** Document the steps of disassembly and the function of each component identified.

**Diagram:** Include a labeled diagram of the computer's internal layout.

**Conclusion:** Discuss how the different components work together to form a functioning computer system.

**Precautions:** Use an antistatic wrist strap to avoid damaging components with static electricity.

**Exercises:** Research the specifications of the CPU and RAM in the system and explain how they affect the computer's performance.



## Workshop 8: Input and Output Devices

**Date:**

**Workshop Number:** 8

**Title:** Input and Output Devices

**Aim:** To understand the role and function of input and output devices in a computer system.

**Objectives:**

1. Identify and connect various input and output devices.
2. Test the functionality of these devices with a computer system.
3. Analyze how these devices interact with the system.

**Significance:** Input and output devices are essential for user interaction with computer systems, and understanding their operation is key to hardware troubleshooting.

**Theoretical Background:** Input devices (e.g., keyboards, mice) allow users to interact with a computer, while output devices (e.g., monitors, printers) provide feedback from the system.

**Equipment:**

- Keyboard, mouse, monitor, printer, etc.
- Computer system

**Observation:** Record the functionality of each device when connected to the computer.

**Diagram:** Provide a schematic showing the connections between the computer and its input/output devices.

**Conclusion:** Explain the importance of input/output devices in the overall functionality of a computer system.

**Precautions:** Ensure that all devices are properly connected to avoid damage or malfunction.

**Exercises:** Compare different types of input devices (e.g., mechanical vs. membrane keyboards) and discuss their advantages and disadvantages.

## Workshop 9: Motherboards and Components

**Date:**

**Workshop Number:** 9

**Title:** Motherboards and Components

**Aim:** To understand the layout and function of the motherboard and its associated components.

**Objectives:**

1. Identify the main components on a motherboard (e.g., CPU socket, RAM slots, PCIe slots).
2. Understand the role of each component in system operation.
3. Assemble a computer system using a motherboard and its components.

**Significance:** The motherboard is the backbone of the computer system, and understanding its layout and components is essential for effective hardware maintenance.

**Theoretical Background:** The motherboard connects all the essential components of a computer, allowing communication between the CPU, RAM, storage, and other peripherals.

**Equipment:**

- Motherboard
- CPU
- RAM
- Power supply
- Screwdriver set

**Observation:** Document the steps taken to assemble the system and any challenges encountered.

**Diagram:** Include a diagram of the motherboard layout, labeling key components.

**Conclusion:** Discuss how the motherboard facilitates communication between the various components in a computer system.

**Precautions:** Ensure that components are installed correctly to avoid damaging the motherboard or other parts.

**Exercises:** Research the differences between various motherboard form factors (e.g., ATX, microATX) and discuss their impact on system design.

## Workshop 10: Resistor Color Coding

**Date:**

**Workshop Number:** 10

**Title:** Resistor Color Coding

**Aim:** To learn and apply the resistor color coding system to identify resistor values.

**Objectives:**

1. Identify resistor values using the color code system.
2. Verify resistor values using a multimeter.
3. Understand the significance of tolerance in resistors.

**Significance:** Accurate identification of resistor values is crucial in circuit design and troubleshooting.

**Theoretical Background:** The resistor color code system uses colored bands to represent numerical values, making it easy to identify resistor values at a glance.

**Equipment:**

- Assorted resistors
- Multimeter
- Resistor color code chart

**Observation:** Record the identified and measured values for various resistors and compare them.

**Diagram:** Include a color code chart for quick reference.

**Conclusion:** Explain the importance of correctly identifying resistor values in circuit assembly and maintenance.

**Precautions:** Handle resistors carefully to avoid damage to the color bands.

**Exercises:** Calculate the resistance value and tolerance of a given set of resistors and verify them with a multimeter.